

**THE UNIVERSITY OF DANANG
UNIVERSITY OF SCIENCE AND TECHNOLOGY
Faculty of Advanced Science and Technology**



LABORATORY REPORT

INTRODUCTION TO VERY LARGE SCALE INTEGRATION IC DESIGN

Instructor : Nguyen Van Cuong

Class : 21ECE

Student : Tran Hoang Minh

Da Nang, September 3rd 2024

Index

I.	Overview of Microwind and DSCH:.....	3
II.	Technical design.....	4
1.	Requirement Specification:.....	4
III.	Logic design.....	5
1.	Top-level Interfaces:	7
2.	Verilog:.....	7
IV.	Circuit design.....	8
1.	Schematic.....	8
2.	Waveform	9
V.	Physical design	10
1.	Design Reference Invertor	10
2.	Layout	14
VI.	Result	16
VII.	Reference.....	17

I. Overview of Microwind and DSCH:

Microwind is a tool for designing and simulating circuits at layout level. The tool features full editing facilities (copy, cut, past, duplicate, move), various views (MOS characteristics, 2D cross section, 3D process viewer), and an analog simulator.

DSCH is software for logic design. Based on primitives, a hierarchical circuit can be built and simulated. It also includes delay and power consumption evaluation.

Silicon is for 3D display of the atomic structure of silicon, with emphasis on the silicon lattice, the dopants, and the silicon dioxide.

The Microwind software works is based on a lambda grid, not on a micro grid. Consequently, the same layout may be simulated in any CMOS technology. The value of lambda is half the minimum polysilicon gate length. Table A-xxx gives the correspondence between lambda and micron for all CMOS technologies available in the companion CD-ROM.

Technology file available in the CD-Rom	Minimum gate length	Value of lambda
Cmos12.rul	1.2 μm	0.6 μm
Cmos08.rul	0.7 μm	0.35 μm
Cmos06.rul	0.5 μm	0.25 μm
Cmos035.rul	0.4 μm	0.2 μm
Cmos025.rul	0.25 μm	0.125 μm
Cmos018.rul	0.2 μm	0.1 μm
Cmos012.rul	0.12 μm	0.06 μm
Cmos90n.rul	0.1 μm	0.05 μm
Cmos70n.rul	0.07 μm	0.035 μm
Cmos50n.rul	0.05 μm	0.025 μm

Table I-xxx: correspondence between technology and the value of lambda in μm

II. Technical design

DESIGN PROJECT

Design, lay out, and simulate a CMOS four-input XOR gate in the standard 0.25 micron CMOS process. You can choose any logic circuit style, and you are free to choose how many stages of logic to use: you could use one large logic gate or a combination of smaller logic gates. The supply voltage is set at 2.5 V! Your circuit must drive an external 20 fF load in addition to whatever internal parasitics are present in your circuit.

The primary design objective is to minimize the propagation delay of the worst-case transition for your circuit. The secondary objective is to minimize the area of the layout. At the very worst, your design must have a propagation delay of no more than 0.5 ns and occupy an area of no more than 500 square microns, but the faster and smaller your circuit, the better. Be aware that, when using dynamic logic, the precharge time should be made part of the delay.

The design will be graded on the magnitude of $A \times t_p^2$, the product of the area of your design and the square of the delay for the worst-case transition.


1. Requirement Specification:

Name	4-input XOR gate
Process	0.25-micron
Supply voltage	2.5V
Propagation delay	< 0.5 ns
Area	< 500 square microns
External load	20 fF

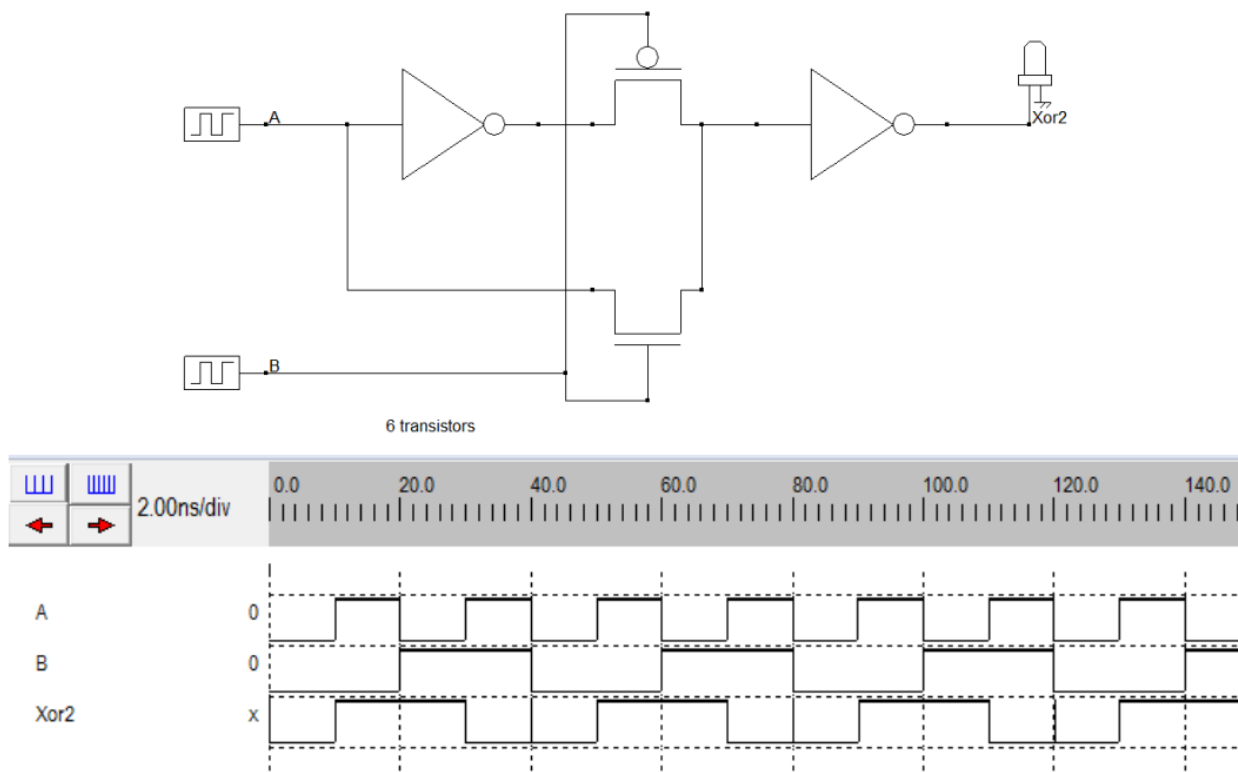III. Logic design

The XOR (Exclusive OR) gate is a digital logic gate that outputs true or high only when the two binary bit inputs to it are unequal. In other words, it outputs a 1 when the number of 1's inputs is odd, making it essential for arithmetic functions in computers and other digital systems.


The 6-transistor XOR gate design is a very compact solution for implementing the XOR function. The schematic diagram is shown in Figure 1. The main drawback is the use of pass transistors which may create non-ideal logic levels due to threshold voltage degradation. In short, n-channel transistors cannot transfer the level 1 correctly, the p-channel transistors cannot transfer the level 0 correctly. Other values are correctly executed. Using DSCH, the observed simulation is always correct, as DSCH do not take into account “weak-1” and “weak-0” levels



The compilation of the XOR gate using Microwind leads to a compact layout, but the non-ideal internal levels do not induce a correct inverter simulation, which creates important negative effects:

- Very large delays
- Important static consumption

Input A	Input B	Input C	Input D	Output Y
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

 

$$\text{OUT} = A \oplus B \oplus C \oplus D = (A \oplus B) \oplus (C \oplus D)$$

1. Top-level Interfaces:

Inputs	Outputs
A	output
B	
C	
D	

2. Verilog:

```
// DSCH3
// 10/20/2024 4:17:22 PM
// D:\download\VLSI1\DSCH1\DSCH\examples\xor4_lan3.sch



module xor4( B,A,C,D,output);
input B,A,C,D;
output output;
wire w5,w6;;
xor #(16) xor2_1(w5,C,D);
xor #(16) xor2_2(output,w6,w5);
xor #(16) xor2_3(w6,A,B);
endmodule

// Simulation parameters in Verilog Format
always
#2000 B=~B;
#1000 A=~A;
#4000 C=~C;
#8000 D=~D;


// Simulation parameters
// B CLK 20.000 20.000
// A CLK 10.00 10.00
// C CLK 40.000 40.000
// D CLK 80.000 80.000
```

IV. Circuit design

1. Schematic

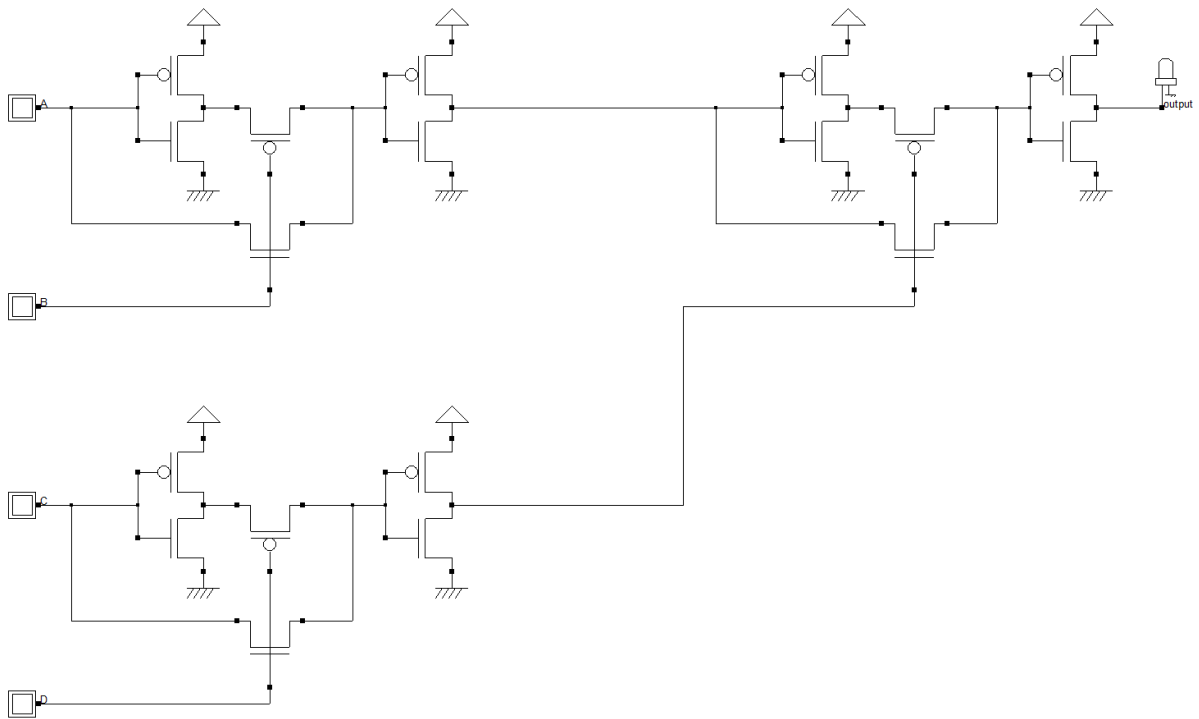 

2. Waveform

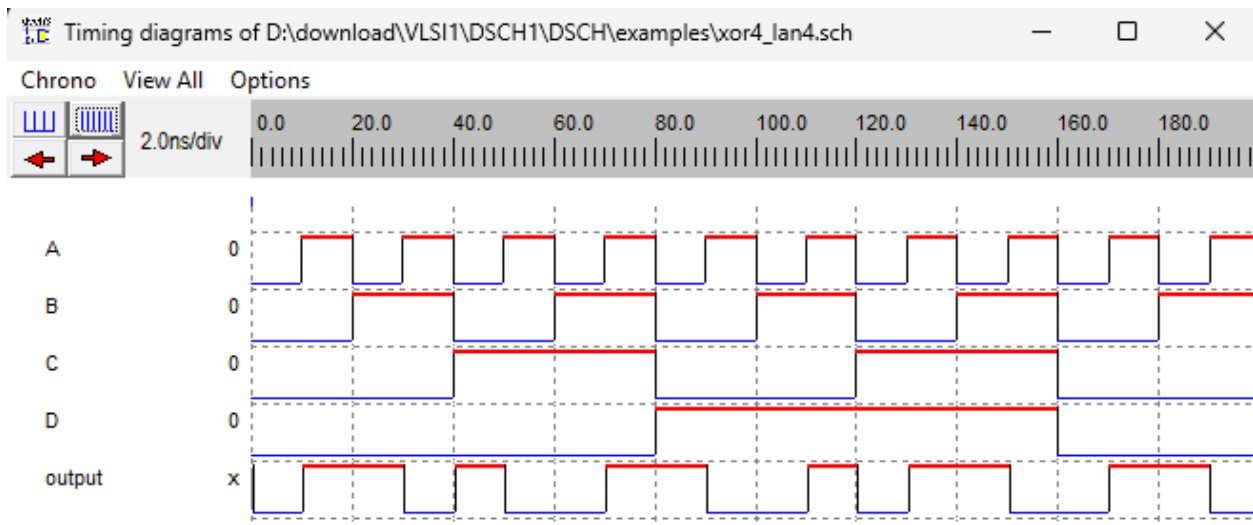

V. Physical design

1. Design Reference Invertor

Design Data — Transistor Model for Manual Analysis

Table 3.2 tabulates the obtained parameter values for the minimum-sized NMOS and a similarly sized PMOS device in our generic 0.25 μm CMOS process. These values will be used as generic model-parameters in later chapters.

Table 3.2 Parameters for manual model of generic 0.25 μm CMOS process (minimum length device).

	V_{T0} (V)	γ ($\text{V}^{0.5}$)	V_{DSAT} (V)	k' (A/V^2)	λ (V^{-1})
NMOS	0.43	0.4	0.63	115×10^{-6}	0.06
PMOS	-0.4	-0.4	-1	-30×10^{-6}	-0.1

From Eq. (5.2), we can derive the required ratio of PMOS versus NMOS transistor sizes such that the switching threshold is set to a desired value V_M . When using this expression, please make sure that the assumption that both devices are velocity-saturated still holds for the chosen operation point.

$$\frac{(W/L)_p}{(W/L)_n} = \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_{DD} - V_M + V_{Tp} + V_{DSATp}/2)} \quad (5.5)$$

So we have $\frac{(W/L)_p}{(W/L)_n} = \frac{115 \times 10^{-6}}{-30 \times 10^{-6}} \times \frac{0.63}{-1} \times \frac{2.50 - 0.43 - \frac{0.63}{2}}{2.50 - 0.4 - \frac{1.0}{2}} = 3.5 \approx 3$

Design Data — MOS Transistor Capacitances

Table 3.5 summarizes the parameters needed to estimate the parasitic capacitances of the MOS transistors in our generic 0.25 μm CMOS process.

Table 3.5 Capacitance parameters of NMOS and PMOS transistors in 0.25 μm CMOS process.

	C_{ox} (fF/ μm^2)	C_O (fF/ μm)	C_j (fF/ μm^2)	m_j	ϕ_b (V)	C_{jsw} (fF/ μm)	m_{jsw}	ϕ_{bsw} (V)
NMOS	6	0.31	2	0.5	0.9	0.28	0.44	0.9
PMOS	6	0.27	1.9	0.48	0.9	0.22	0.32	0.9

Table 5.2 Components of C_L (for high-to-low and low-to-high transitions).

Capacitor	Expression	Value (fF) (H→L)	Value (fF) (L→H)
C_{gd1}	$2\ CGD0_n\ W_n$	0.23	0.23
C_{gd2}	$2\ CGD0_p\ W_p$	0.61	0.61
C_{db1}	$K_{eqn}\ AD_n\ CJ + K_{eqsw_n}\ PD_n\ CJSW$	0.66	0.90
C_{db2}	$K_{eqp}\ AD_p\ CJ + K_{eqsw_p}\ PD_p\ CJSW$	1.5	1.15
C_{g3}	$(CGD0_n + CGSO_n)\ W_n + C_{ox}\ W_n\ L_n$	0.76	0.76
C_{g4}	$(CGD0_p + CGSO_p)\ W_p + C_{ox}\ W_p\ L_p$	2.28	2.28
C_w	From Extraction	0.12	0.12
C_L	Σ	6.1	6.0

$$C_{int} = C_{gd1} + C_{gd2} + C_{db1} + C_{db2}$$

$$C_{int} = 2CGD0_n W_n + 2CGD0_p W_p + C_{db1} + C_{db2}$$

$$C_{int} = 2 \times 0.31 \times W_n + 2 \times 0.27 \times W_p + 0.66 + 1.5$$

$$C_{int} = 0.62 \times W_n + 0.54 \times W_p + 2.16$$

$$\text{We have } C_L = C_{int} + C_{ext}$$

From the requirement with external load is equal 20 fF, so

$$C_L = C_{int} + C_{ext} = (0.62 \times W_n + 0.54 \times W_p + 2.16) + 20$$

Design Data — Equivalent Resistance Model

Table 3.3 enumerates the equivalent resistances obtained by simulation of our generic 0.25 μm CMOS process. These values will come in handy when analyzing the performance of CMOS gates in later chapters.

Table 3.3 Equivalent resistance R_{eq} ($W/L=1$) of NMOS and PMOS transistors in 0.25 μm CMOS process (with $L = L_{min}$). For larger devices, divide R_{eq} by W/L .

V_{DD} (V)	1	1.5	2	2.5
NMOS (k Ω)	35	19	15	13
PMOS (k Ω)	115	55	38	31

And with the generic 0.25 μm CMOS process, we have the R_{eq} for NMOS and PMOS at $V_{DD}=2.5\text{ V}$ is:

$$R_{eqn} = 13\text{ k}\Omega \text{ and } R_{eqp} = 31\text{ k}\Omega$$

And with the requirement for propagation delay is $< 0.5\text{ ns}$.

$$t_p = 0.69C_L \left(\frac{R_{eqn} + R_{eqp}}{2} \right) < 0.5\text{ ns}$$

$$t_p = 0.69[0.62 W_n + 0.54 W_p + 2.16 + 20] \left(\frac{R_{eqn} + R_{eqp}}{2} \right) < 0.5\text{ ns}$$

$$\Rightarrow 0.69[0.62 \times W_n + 0.54 \times W_p + 2.16 + 20] \left(\frac{13\text{ k}\Omega + 31\text{ k}\Omega}{2} \right) < 0.5\text{ ns}$$

$$\Rightarrow 0.62 \times W_n (\text{fF}) + 0.54 \times W_p (\text{fF}) < 10.8 (\text{fF})$$

$$\text{And we have } \frac{\left(\frac{W}{L}\right)_p}{\left(\frac{W}{L}\right)_n} \approx 3 \text{ or } W_p = 3W_n$$


$$\Rightarrow W_p < 17.277\text{ }\mu\text{m} \text{ and } W_n < 5.750\text{ }\mu\text{m} \text{ and } W_p = 3W_n$$

Choose $W_p = 2.500\text{ }\mu\text{m}$ and $W_n = 0.750\text{ }\mu\text{m}$

So, Cint of reference inverter is: $0.62 W_n + 0.54 W_p + 2.16$

$$= 0.62 W_n + 0.54 * W_p + 2.16 = 0.62 * 0.75 + 0.54 * 2.5 + 2.16 = 3.975 \approx 4$$

Design the 4input XOR gate :

 

The method of Logical Effort is applied with the following steps:

$$1. F = CL/C_{int} = 24/4 = 6$$

$$2. G = 4 \times 4 = 16$$

$$3. B = 1$$

$$4. H = GBF = 96, \text{ so the optimal stage effort is } f^* = \sqrt{H} = 9.79$$


$$y = 9.79 * 9.79 / 4 * 4 = 9.79$$

$$x = 9.79 / 2 * 4 = 4.89$$

 5. So the gate sizes are

$$\left(\frac{W}{L}\right)_{n,x} = 1\left(\frac{4.89}{4}\right) \approx 1, \left(\frac{W}{L}\right)_{p,x} = 3\left(\frac{4.89}{4}\right) \approx 3,$$

$$\left(\frac{W}{L}\right)_{n,y} = 1\left(\frac{9.79}{4}\right) \approx 4, \left(\frac{W}{L}\right)_{p,y} = 3\left(\frac{9.79}{4}\right) \approx 12$$



$$\text{The XOR2 gate delay is } d1 = g1h1 + p1 = 4/2 \times 1 + 4 = 6$$

$$d2 = g2h2 + p2 = 4 \times 1 + 4 = 8$$

Hence, the path delay is 14. Recall that delay is expressed in units of τ . In a 0.25-micron process with $\tau = 61\text{ps}$, the delay is 854ps




2. Layout

Size Labels Routing

Mos size (μm)



Width P	2.500
Length P	0.250
Width N	0.750
Length N	0.250



Virtual R,L,C Para... — □ ×

Capa between node and ground

Capacitance value (pF): 0.02


 OK  Cancel

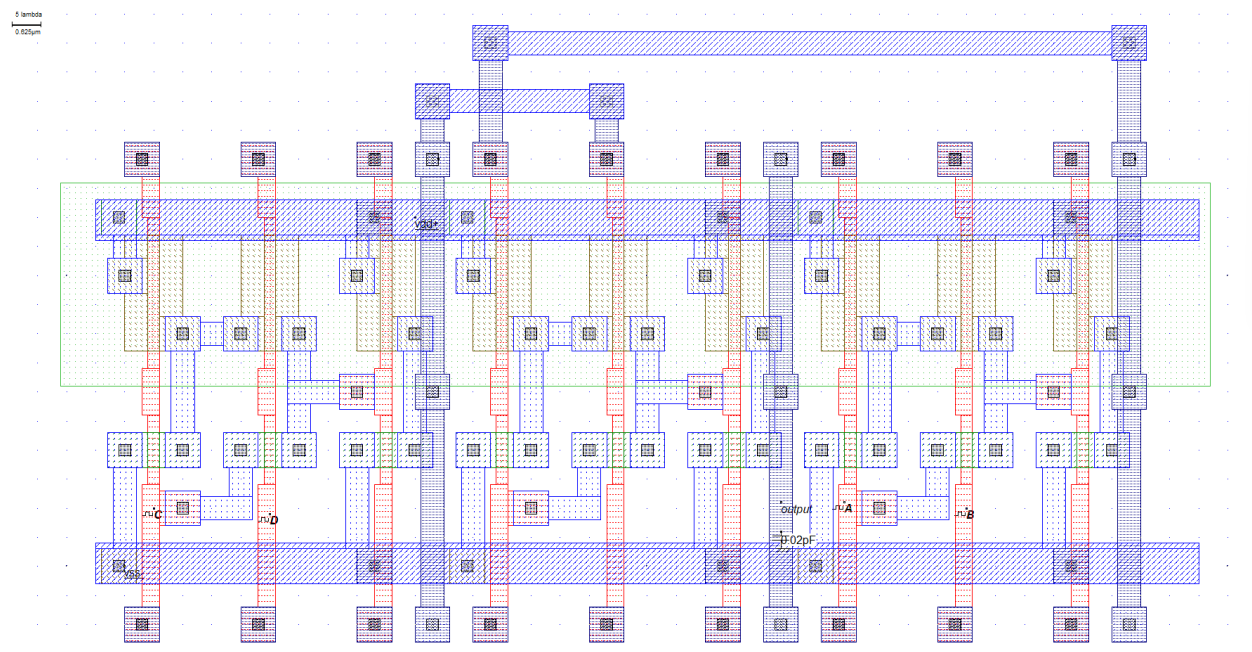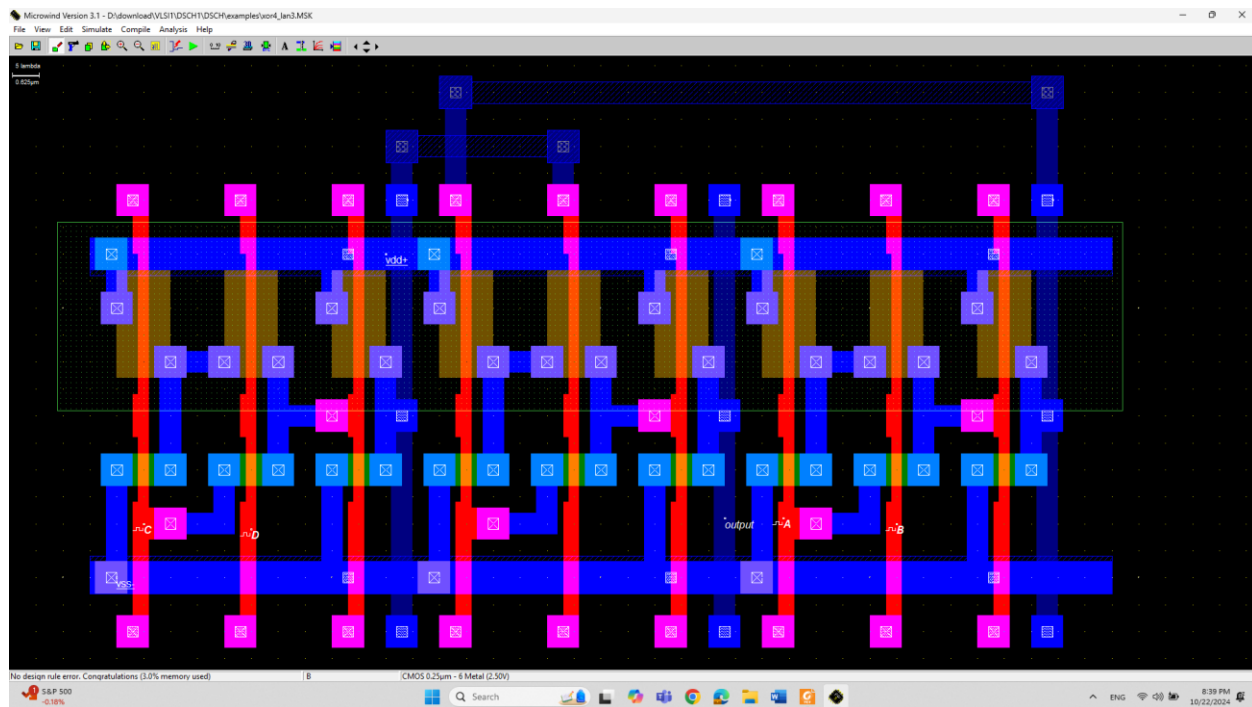

 
VI. Result

Functionality: the waveform observed demonstrates that physical design is functioning correctly as 4-input xor gate.

Speed: Confirm that the propagation delay meets the 0.5 ns specification.



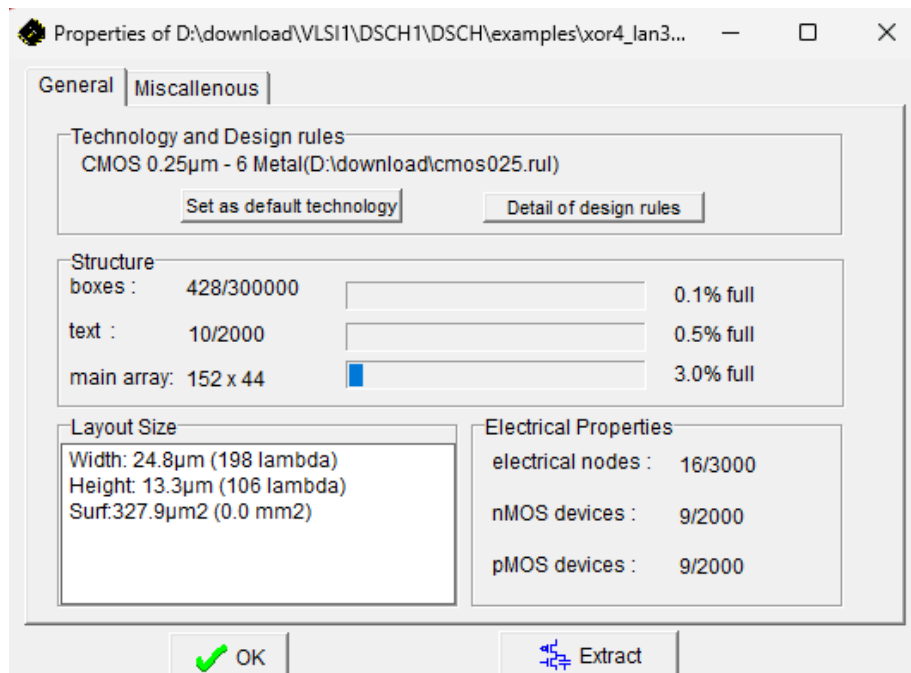Area: Validate that the area is within acceptable limits ($24.8 \times 13.3 = 330$ square microns)



VII. Reference

[Microsoft Word - Book appendixA e.doc](#)

[jntuh vlsi lab - Research is Fun](#)

[Microsoft PowerPoint - MohantyVLSI5Microwind](#)

<https://www.bing.com/ck/a?!&&p=6feccc956365be4c68b9e00ccda95e9aa40e17470bb1d078f7df26e572b0200eJmltdHM9MTczMDUwNTYwMA&ptn=3&ver=2&hsh=4&fclid=3bdf4c52-f7fb-6750-3bff-4348f69d6642&psq=xor+in+microwind&u=a1aHR0cHM6Ly9taWNyb3dpbmQubmV0L2Rvd25sb2FkLzE3&ntb=1>